



KNOW-HOW TO CREATE / AXIOM-IC.COM

HOW THE “DIGITAL” AMPLIFIER BECOMES MORE DIGITAL

Sander Gierkink

Outline

- Introduction
- Class D: the “Digital” Amplifier
- “Digital” vs. More Digital
- Challenges in design of feedback AD converter
- Conclusions

Introduction

Axiom IC: who are we?

- Mixed-signal IC design house
- Specialized in low-power data converters and audio
- Located in Enschede
- Close contacts with University of Twente
- Founded in October 2007
- 20 Employees

Trends in audio

- All audio sources become digital
 - even broadcast radio
- Digital sound processing for “better” sound quality
- Improved fidelity at lower cost
- Car audio: tailored towards specific car acoustics
- Portable audio:
 - higher sound levels for less juice
 - longer battery life
- More channels
 - Home: 5.1, 7.1, 9.1
 - Car: currently 12 channels, going up 20+


⇒ **Need for efficient HiFi power amplifiers**

Reasons for going digital

- More flexibility
- Easier to add features
- Scales with technology
- Cost reduction
- Less sensitive to cross talk
- Automatic layout place and route
- No specialized analog design skills required
- Testability
- Sexy


Current status “digital” amplifier

DA converter moves to the power die

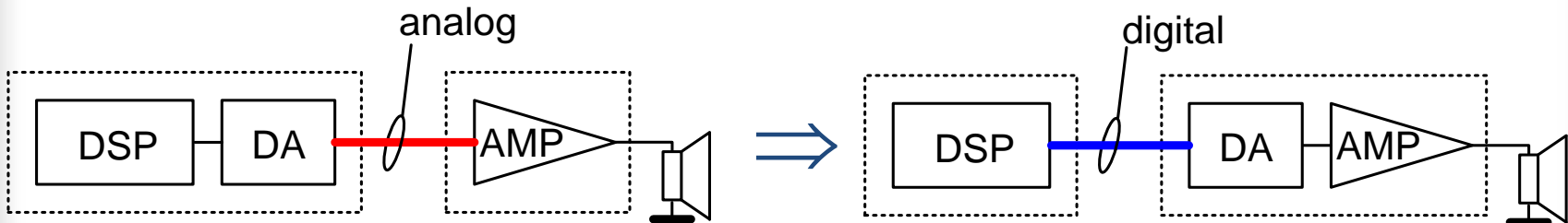


- DSP and amplifier remain on separate die, to allow for aggressive scaling of DSP
- DA converter moves to the power amplifier die
 - made possible by faster CMOS in power technology
 - interface becomes digital:
 - less cross talk problems
 - allows for connecting amps to a bus (in car)

Examples: high power class D

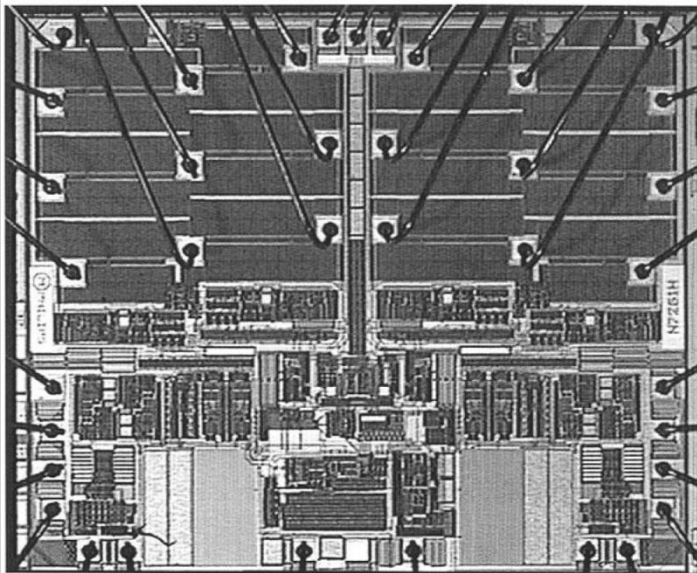

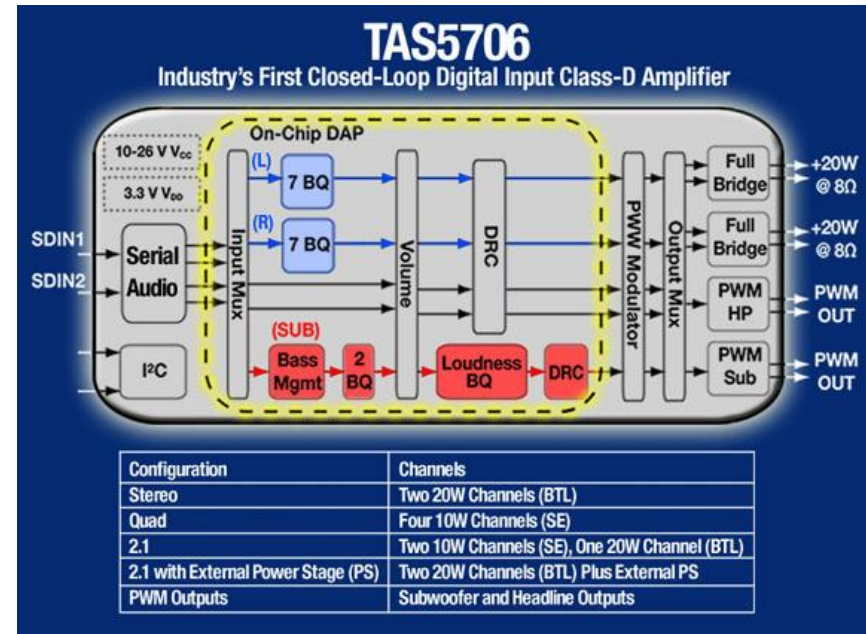- 2x100W Class D; 22mm²
M. Berkhout, NXP, JSSC 2003
- closed loop, PWM
 - analog loop filter
 - analog inputs



- 2x20W Class D
Texas Instruments 2008
- closed loop
 - analog loop filter
 - digital inputs

Where are we headed?

We are headed for a more digital amplifier:

Closed loop amplifier with internal digital gain and digital feedback

Some have claimed the term in the past for:

- Any *analog* amplifier with digital inputs (DA converter at input)
- Open or closed-loop *analog* class D amplifier (“switching is digital”)

⇒ “digital” is often misleading: internally the gain is implemented analog

⇒ Class D does not mean digital

Keep in mind:

the pure digital amplifier does not exist:

the power stage is always analog

Axiom IC

In the past, Axiom IC has developed:

- integrated class AB audio power amplifiers for car audio
- high performance DA converters for amplifiers with digital input



Axiom IC currently develops a closed-loop class D power amplifier featuring:

- Digital inputs
- Digital internal loop filter (internal gain is digital)
- ADC in the feedback path

..such that the internal audio processing is digital
(including gain and feedback)

Class D: the “digital” amplifier

Class D: principle

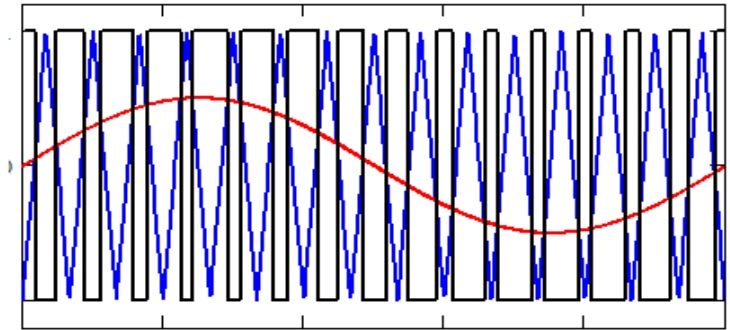
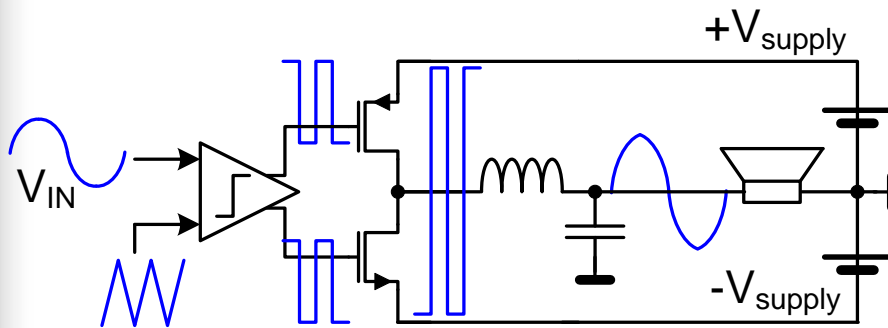


Principle of class D:

- Output stage switches between supply rails
 \Rightarrow Low dissipation in power transistors ($P_{\text{diss}} = V_{\text{DS}} \cdot I_{\text{load}}$)
- Audio modulates the pulse width (“PWM”)
- Requires external reconstruction LC filter

The design and operation of a class D power stage + drivers is analog by nature!

Efficiency comparison

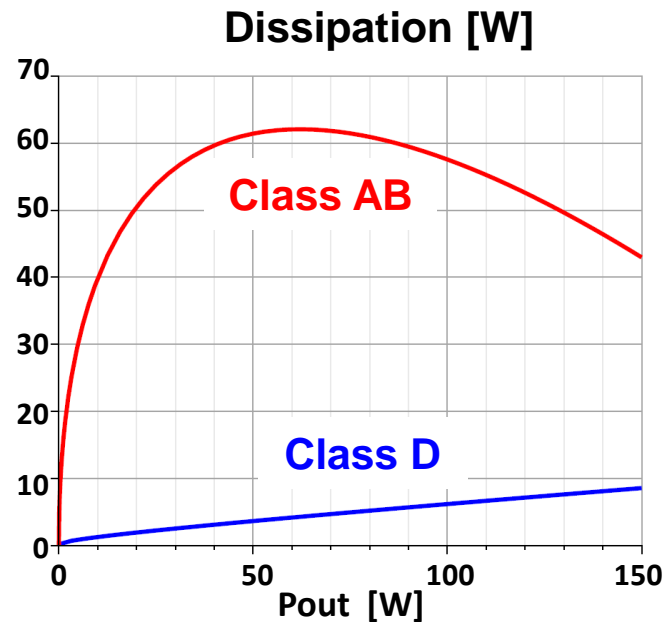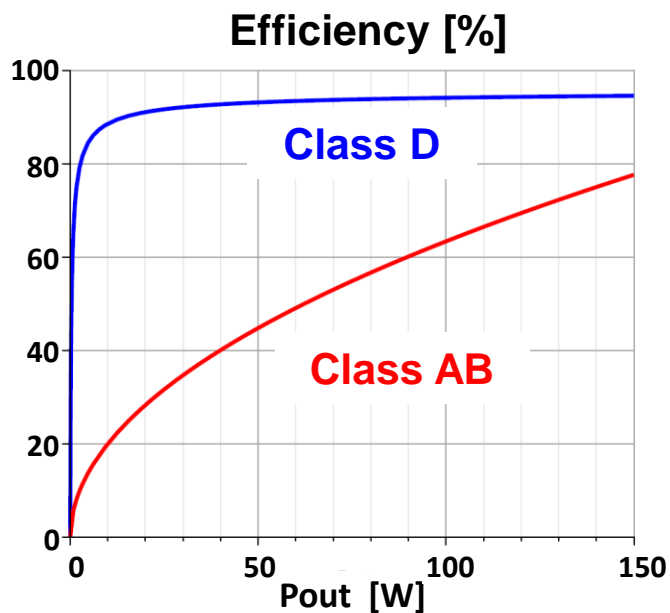


Class AB: linear


Class D: switching

Class D ⇒ smaller heat sink, cheaper IC package,
smaller power supply, extended battery life

Class D: spectral content

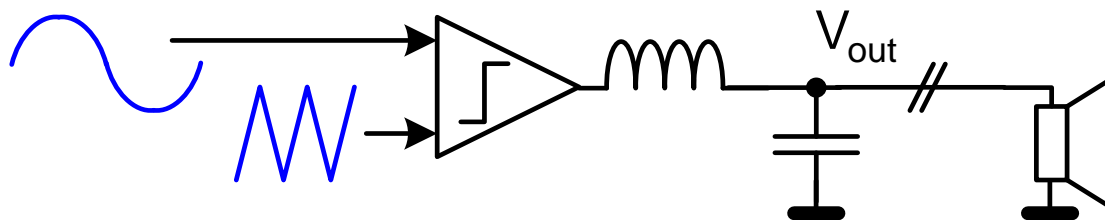


Spectrum of V_{out}

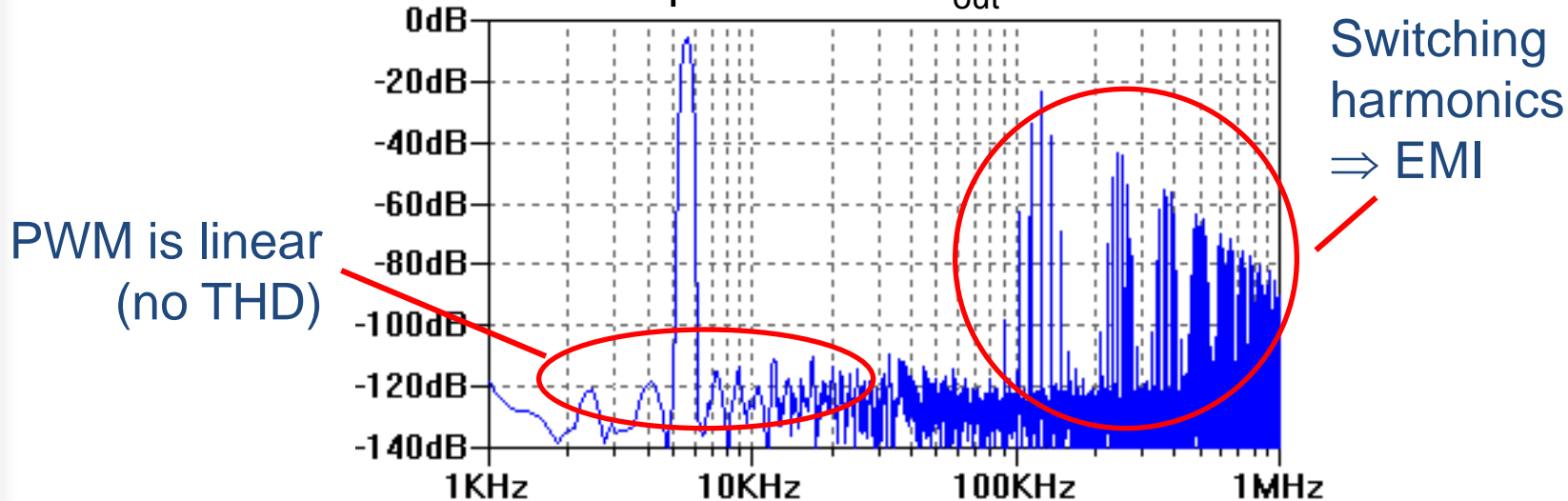

Switching harmonics interfere with AM band (0.5 – 1.5MHz)


Class D: topologies

Open Loop

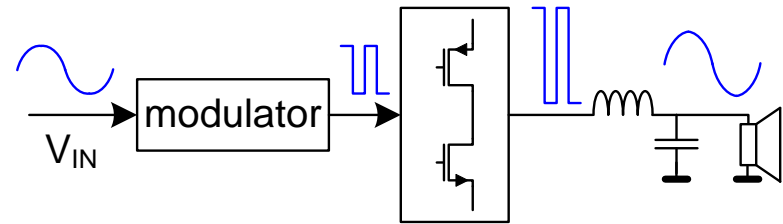


Closed Loop:

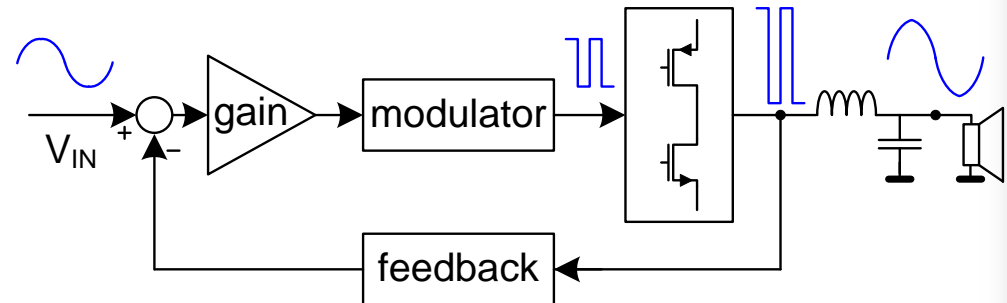
- **Feedback Before Filter**
Most commonly used analog solution nowadays



- **Feedback After Filter (FBAF)**

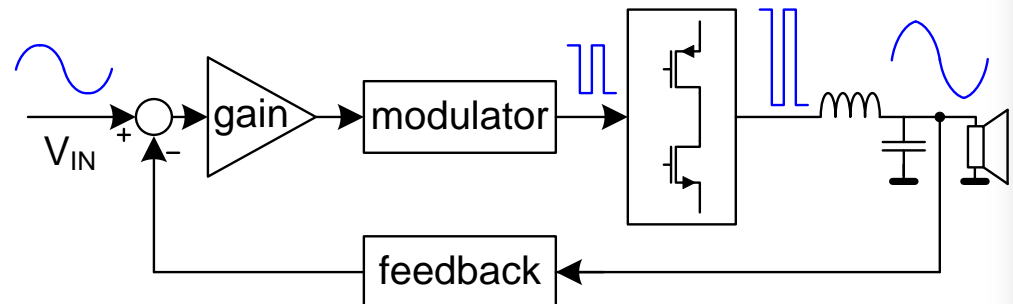

Why closed loop?

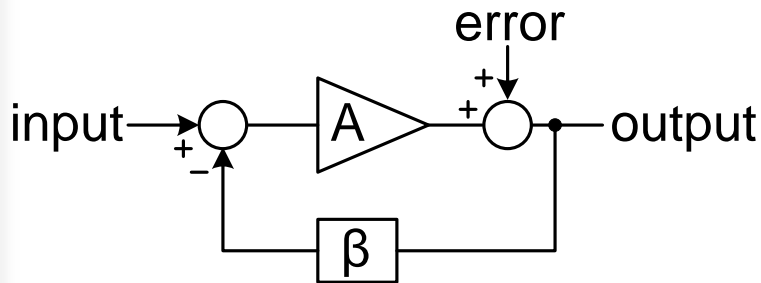


$$\begin{aligned} \text{output} &= \frac{A}{1+A\cdot\beta} \cdot \text{input} + \frac{1}{1+A\cdot\beta} \cdot \text{error} \\ &\approx \frac{1}{\beta} \cdot \text{input} + \frac{1}{A\cdot\beta} \cdot \text{error} \end{aligned}$$

- Assumptions:
- Gain A is large, but inaccurate
 - $A\cdot\beta \gg 1$

- Conclusion:
- ⇒ Make β accurate for well-defined transfer
 - ⇒ Make A large for good error suppression


Open Loop

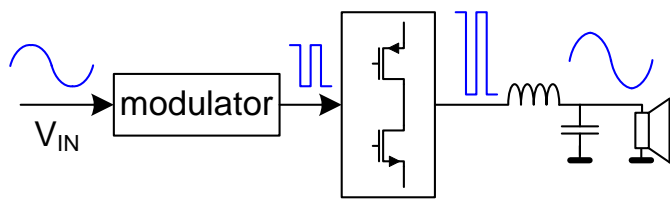

- 😊 Simple
- 😞 No suppression of non-linearity
- 😞 No power supply rejection
- 😞 Requires excellent supply (bulky, cost)

Popular in combination with a digital modulator

Closed Loop

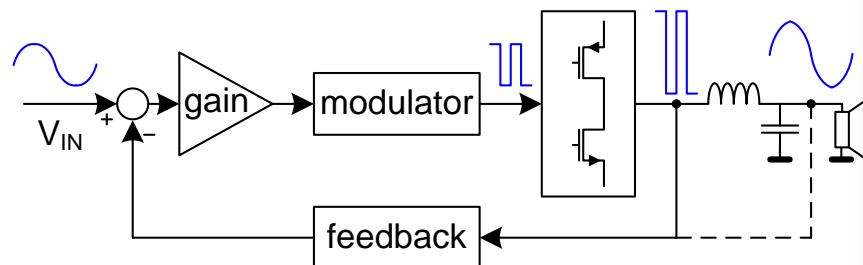


- 😊 Suppression of non-linearity
- 😊 Good power supply rejection
- 😊 With feedback after filter: frequency response independent of speaker impedance

Challenge:
Stability


“Digital” vs. More Digital

“Digital”

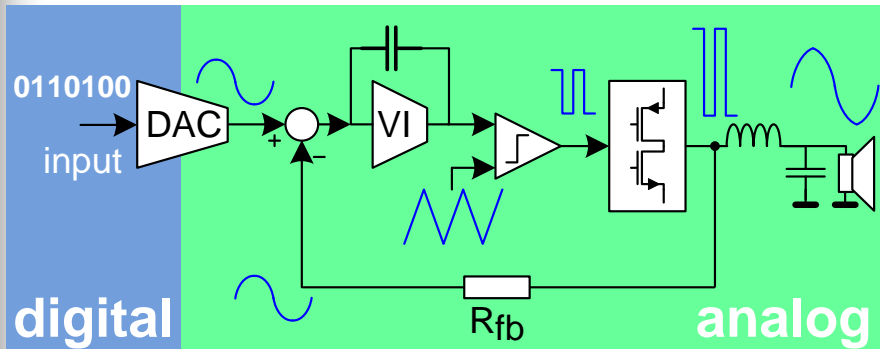


- 😊 Feedback is a simple resistor
- 😊 Proven performance
- 😞 Loop filter requires capacitors (area)
- 😞 Component spread \Rightarrow low order loop filter \Rightarrow average THD
- 😞 Internal analog nodes \Rightarrow sensitive to cross talk

More Digital

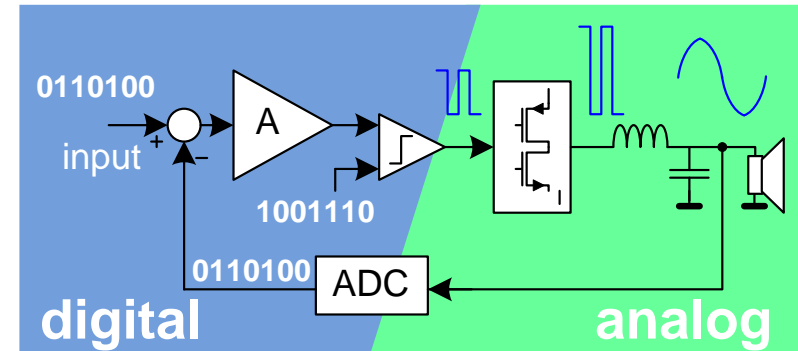

- 😞 Feedback is ADC: not simple
- 😞 Not proven yet: research topic
- 😊 Area efficient
- 😊 No component tolerance \Rightarrow high order loop filter \Rightarrow good THD
- 😊 Internal digital nodes
- 😊 Rapid prototyping (FPGA)
- 😊 Flexible

Analog vs. digital loop gain

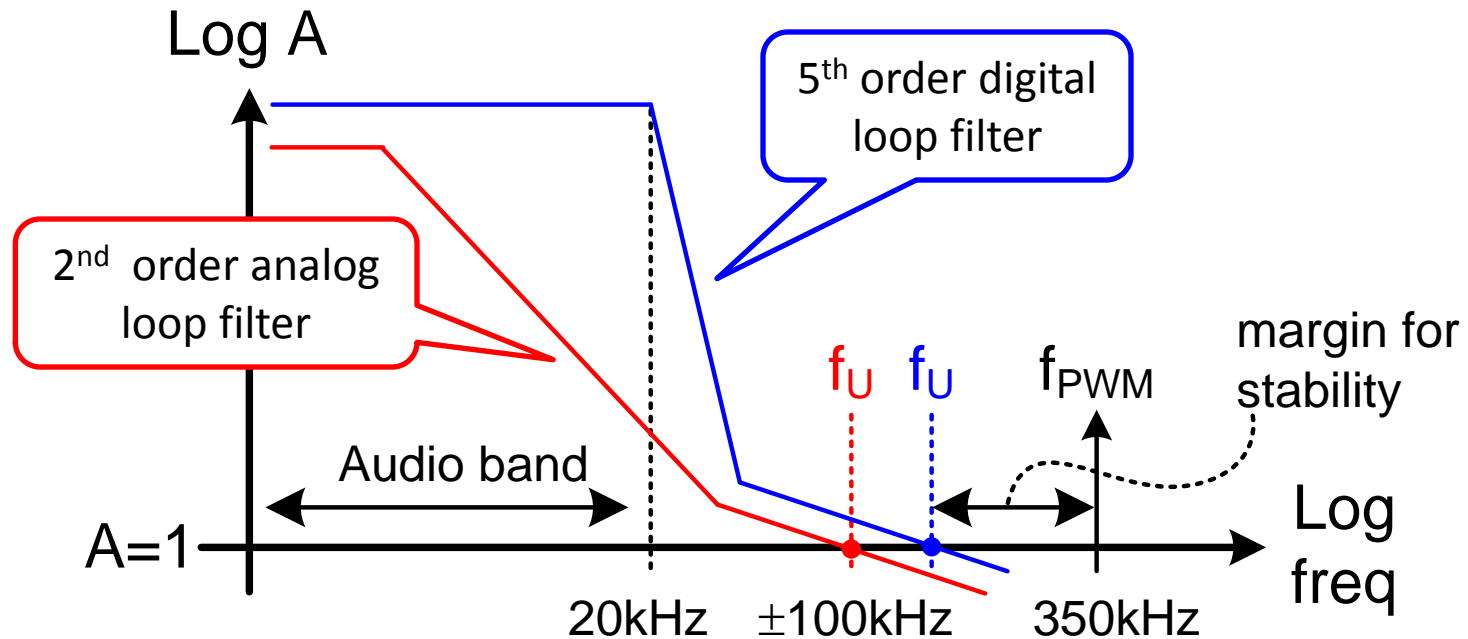


Analog loop filter must be of relative low order,
due to margins for component spread

Digital allows a more aggressive loop filter
⇒ better THD at high audio frequencies

Feedback ADC

Feedback ADC

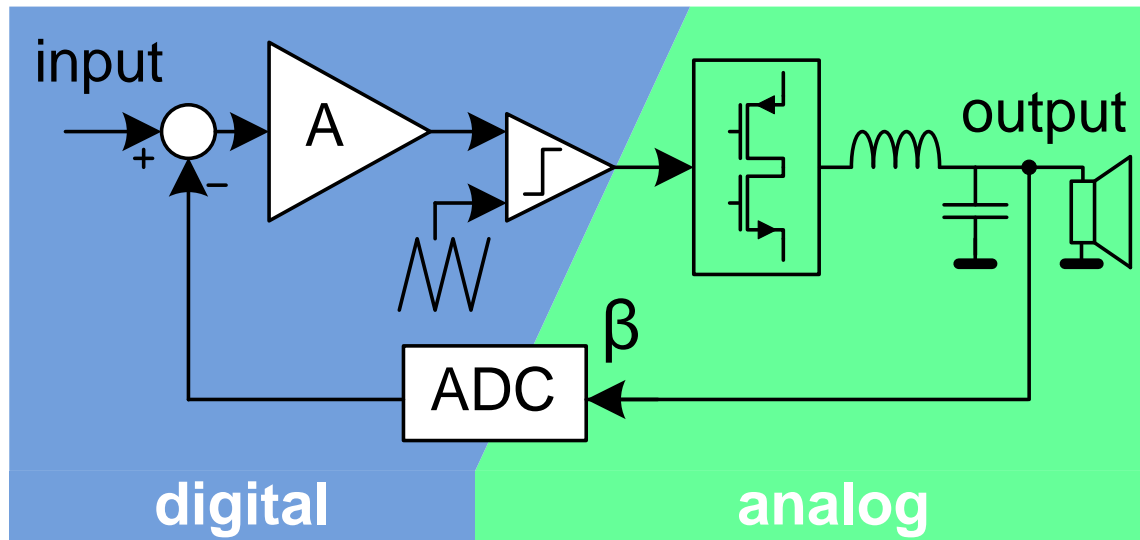

$$\text{output} = \frac{A}{1+A \cdot \beta} \cdot \text{input} \approx \frac{1}{\beta} \cdot \text{input}$$

ADC is in feedback path and determines performance of overall system!

Feedback ADC

Requirements:

- High signal-to-noise and low distortion: 120dB audio dynamic range
⇒ sigma delta
- Low out-of-band noise: to avoid down mixing in PWM modulator
⇒ additional internal filtering
- Low latency (for loop stability): delay \ll 1 PWM cycle
⇒ conflicts with filtering

Risks:

- Supply & substrate bounce: ADC on same die as power stage!
⇒ Design must be fully differential with good CMRR

Conclusions

- The term “digital” amplifier is quite misleading:
at best, it refers to an analog amplifier with DA converter @ input
- Axiom IC currently develops a more digital amplifier featuring a digital loop filter and feedback ADC:
 - More aggressive loop filter possible \Rightarrow lower THD
 - More flexible than analog
 - Fewer interference-sensitive analog nodes
- The feedback ADC is the most critical part:
 - Will determine overall performance
 - Challenge: low latency, low HF quantization noise



KNOW-HOW TO CREATE / AXIOM-IC.COM